

Logic Gates & Logic Families



Logic Gates: Symbol, diode/transistor switch circuit and logical expression, truth table of basic gates (AND, OR, NOT), Universal gates (NAND, NOR) and special purpose gates (Ex-OR, Ex-NOR), Tristate Logic.



Boolean Algebra: Laws of Boolean algebra, Duality Theorem, De-Morgan's Theorem

Logic Gates & Logic Families

Logic Gates & Logic Families



Logic Gates: Symbol, diode/transistor switch circuit and logical expression, truth table of basic gates (AND, OR, NOT), Universal gates (NAND, NOR) and special purpose gates (Ex-OR, Ex-NOR), Tristate Logic.



Boolean Algebra: Laws of Boolean algebra, Duality Theorem, De-Morgan's Theorem



Logic Families: Characteristics of Logic families: Noise Margin, Power Dissipation, Figure of merit, Fan in and Fan out, Speed of operation, Comparison TTL, CMOS, Types of TTL NAND gate.

Basics.....



Logic gates are the fundamental building blocks of digital systems.



The name logic gate is derived from the ability of such devices to make decisions, in the sense

that it produces one output level when some combinations of input levels are present



Inputs & Outputs for Logic Circuits



Input & Output of logic gates can occur only in two levels.

HIGH

True

ON

1

LOW

False

OFF

0

Basics.....

Truth Table




A table which lists all the possible combinations of input variables and the corresponding outputs is called a “Truth Table”.



It shows how the logic circuits output responds to various combinations of logic levels at the inputs

Switches in parallel => OR

 

Switch 1	Switch 2	Output
OFF	OFF	OFF
OFF	ON	GLOW
ON	OFF	GLOW
ON	ON	GLOW

Basics.....



Logic



A logic in which the voltage levels represent logic 1 and logic 0.



Level logic may be Positive or Negative.



A **“Positive Logic”** is the one which the higher of the two voltage levels represents the logic 1 and the lower of the two voltage level represents the logic 0.



A **“Negative Logic”** is the one which the lower of the two voltage levels represents the logic 1 and the higher of the two voltage level represents the logic 0.

Basics.....



Logic



Positive Logic

Logic 0 (LOW)=0V

Logic 1 (HIGH)=+5V




Negative Logic

Logic 0 (LOW)=+5V

Logic 1 (HIGH)=0V


Logic Gates

Logic Gates

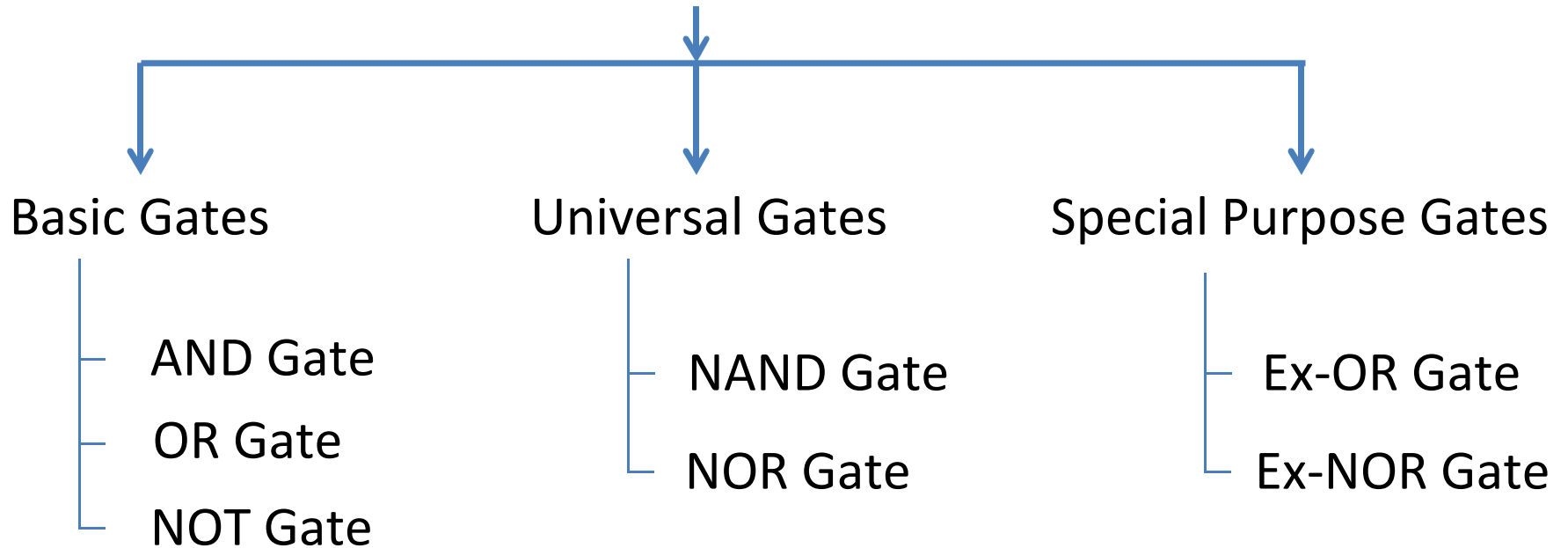


AND Gate

 - ✓ An AND gate has two or more inputs but only one output.
- ✓ The output assumes the logic 1 state, when both inputs are at logic 1 state.
- ✓ The output assumes the logic 0 state even if one of its inputs is at logic 0 state.




AND Gate

 


Inputs		Output
A	B	$Y=A.B$
0	0	0

AND Gate

 


Inputs		Output
A	B	$Y=A.B$
0	0	0
0	1	0

AND Gate

 

Inputs		Output
A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0


AND Gate

 


Inputs		Output
A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1

3 - Input AND Gate

 3 – Input AND Gate using 2 – Input AND Gate




Symbol : 3 – Input AND Gate

 

Truth Table : 3 – Input AND Gate

Input			Output $Y = A.B.C$
A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

 AND Gate IC – IC 7408 (Quad 2 I/P AND Gate)



Pin Configuration of IC 7408



This device contains four independent gates each of which performs the logic AND function.

$$Y = AB$$


Inputs		Output
A	B	Y
L	L	L
L	H	L
H	L	L
H	H	H

H = High Logic Level

L = Low Logic Level


Function Table of IC 7408

Verification of AND Gate IC 7408

 


Verification of AND Gate IC 7408

 Double check the pin numbers when working with ICs.




Verification of AND Gate IC 7408

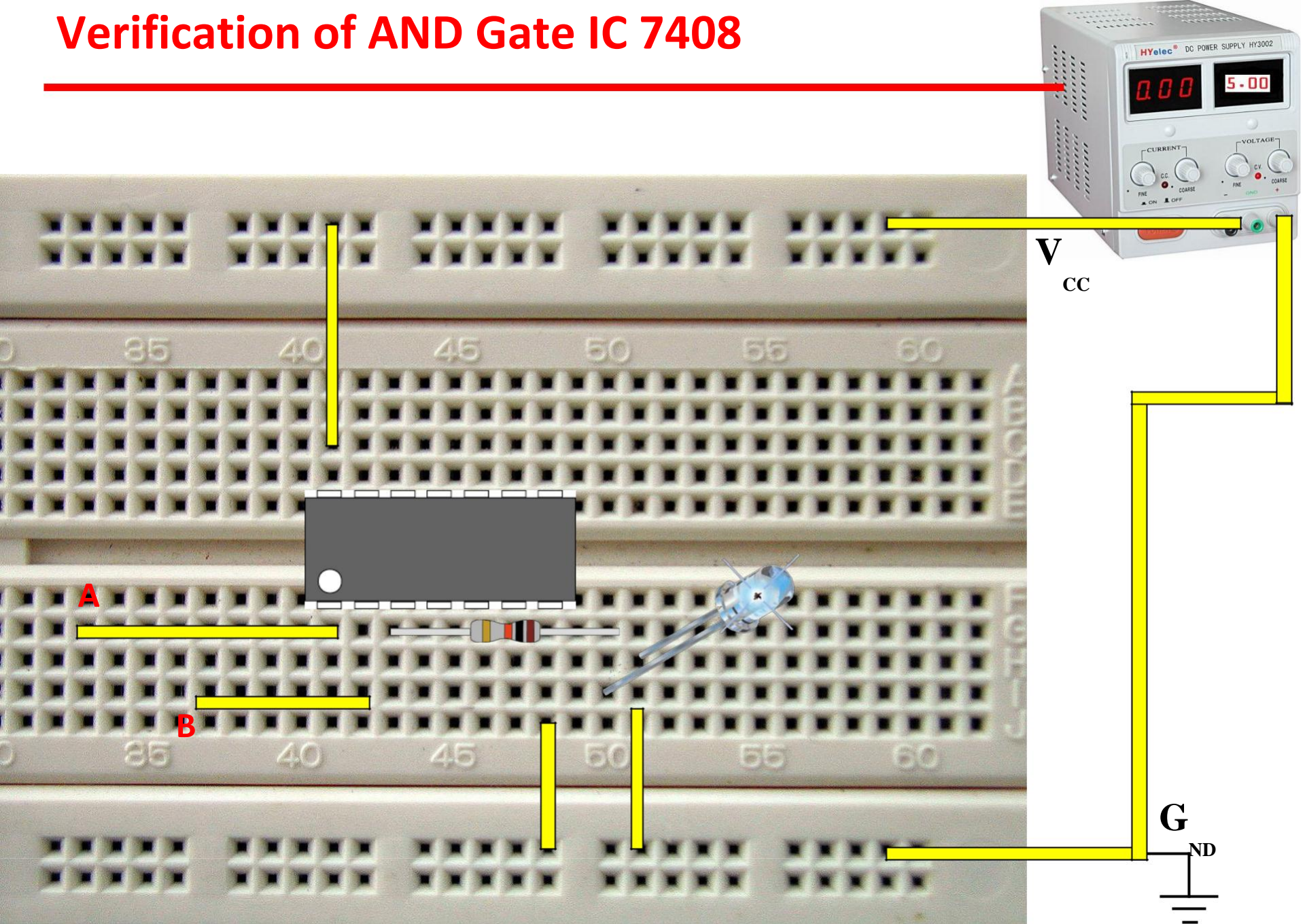


OR Gate

 - ✓ An OR gate has two or more inputs but only one output.
- ✓ The output assumes the logic 1 state, when even if one of its inputs is in logic 1 state.
- ✓ The output assumes the logic 0 state only when both the inputs are in logic 0 state.




OR Gate

 

$Y=A+B$
0


Inputs		Output
A	B	$Y=A+B$
0	0	0

OR Gate

 


Inputs		Output
A	B	$Y=A+B$
0	0	0
0	1	1

OR Gate

 

Inputs		Output
A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1


OR Gate

 


Inputs		Output
A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1
1	1	1

Three Input OR Gate

 3 – Input OR Gate using 2 – Input OR Gate




Symbol : 3 – Input OR Gate

 

Truth Table : 3 – Input OR Gate

Input			Output $Y = A + B + C$
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 OR Gate IC – IC 7432 (Quad 2 I/P OR Gate)



Pin Configuration of IC 7432



This device contains four independent gates each of which performs the logic OR function

$$Y = A + B$$

Inputs		Output
A	B	Y
L	L	L
L	H	H
H	L	H
H	H	H


H = High Logic Level

L = Low Logic Level


Function Table of IC 7432

NOT Gate (Inverter)

 - ✓ A NOT gate, also called inverter, has only one input and of course only one output.
- ✓ It is a device whose output is always the complement of its input.
- ✓ That is, the output of a NOT gate assumes the logic 1 state when its input is in logic 0 state and vice versa.




NOT Gate

 

Input	Output
A	$Y = \bar{A}$
0	1

NOT Gate

 

Input	Output
A	$Y = \bar{A}$
0	1
1	0

Unit II – Logic Gates & Logic Families



Logic Gates: Symbol, diode/transistor switch circuit and logical expression, truth table of basic gates (AND, OR, NOT), Universal gates (NAND, NOR) and special purpose gates (Ex-OR, Ex-NOR), Tristate Logic.



Boolean Algebra: Laws of Boolean algebra, Duality Theorem, De-Morgan's Theorem



Logic Families: Characteristics of Logic families: Noise Margin, Power Dissipation, Figure of merit, Fan in and Fan out, Speed of operation, Comparison TTL, CMOS, Types of TTL NAND gate.


Universal Gates (NAND and NOR Gate)

- ✓ NAND and NOR gates are Universal Gates.
- ✓ Both NAND and NOR gates can perform all the three basic logic functions (AND, OR and NOT).
- ✓ Therefore, AOI logic can be converted to NAND logic or NOR logic



NAND Gate

✓
NAND means NOT AND i.e. AND output is inverted.

 ✓
So NAND gate is a combination of an AND gate and a NOT gate.




AND Gate NOT Gate

  

NAND Gate


NAND Gate

 - ✓ The output is logic 0 level, only when all the inputs are logic 1 level.
- ✓ For any other combination of inputs, the output is a logic 1 level.




Logic Symbol

NAND Gate

 


Inputs		Output
A	B	$Y = \overline{A \cdot B}$
0	0	1

NAND Gate

 


Inputs		Output
A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1

NAND Gate

 


Inputs		Output
A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1

NAND Gate

 


Inputs		Output
A	B	$Y = \overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0

3 - Input NAND Gate

 

INPUT			OUTPUT
A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

 NAND Gate IC – IC 7400 (Quad 2 I/P NAND Gate)



Pin Configuration of IC 7400



This device contains four independent gates each of which performs the logic NAND function.

$$Y = \overline{AB}$$

Inputs		Output
A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L


H = HIGH Logic Level

L = LOW Logic Level

Function Table of IC 7400


NOR Gate

 - ✓ NOR means NOT OR i.e. OR output is inverted.
- ✓ So NOR gate is a combination of an OR gate and a NOT gate.




NOR Gate

 - ✓ The output is logic 1 level, only when all the inputs are logic 0 level.
- ✓ For any other combination of inputs, the output is a logic 0 level.




Logic Symbol

NOR Gate

 


Inputs		Output
A	B	$Y = \overline{A+B}$
0	0	1

NOR Gate

 


Inputs		Output
A	B	$Y = \overline{A + B}$
0	0	1
0	1	0

NOR Gate

 


Inputs		Output
A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0

NOR Gate

 


Inputs		Output
A	B	$Y = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

3 – Input NOR Gate

 

INPUT			OUTPUT
A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 NOR Gate IC – IC 7402 (Quad 2 I/P NOR Gate)



Pin Configuration of IC 7402



This device contains four independent gates each of which performs the logic NOR function.

$$Y = \overline{A + B}$$

Inputs		Output
A	B	Y
L	L	H
L	H	L
H	L	L
H	H	L



H = HIGH Logic Level

L = LOW Logic Level

Function Table of IC 7402



Universal Gate

NOT Gate using NAND Gate

  

Universal Gate



AND Gate using NAND Gate

  

$$Y = A.B \because \overline{\overline{A}} = A$$

Universal Gate

OR Gate using NAND Gate

  



$$Y = \overline{\bar{A} \cdot \bar{B}}$$

$$Y = A + B$$

(\because Demorgan's Theorem)



Universal Gate

NOR Gate using NAND Gate

  



Universal Gate

NOT Gate using NOR Gate

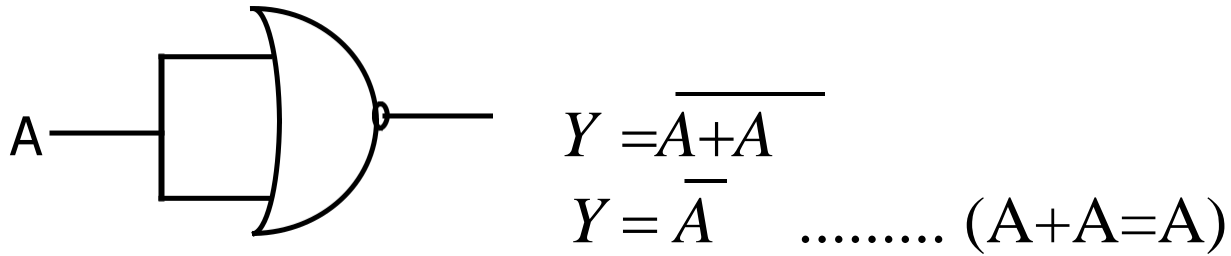 


Universal Gate

OR Gate using NOR Gate

  


Universal Gate

AND Gate using NOR Gate

 

$$Y = \overline{\overline{A} + \overline{B}}$$



$$Y = A.B$$

 



(\because Demorgan's Theorem)

Universal Gate

NAND Gate using NOR Gate

  

Why NAND Logic or NOR Logic?

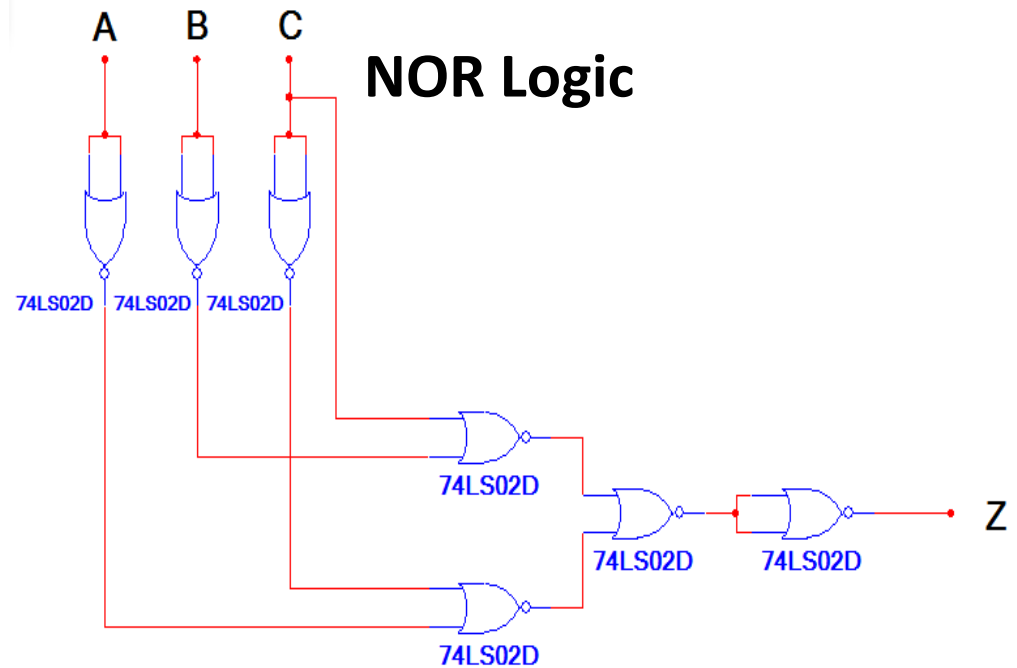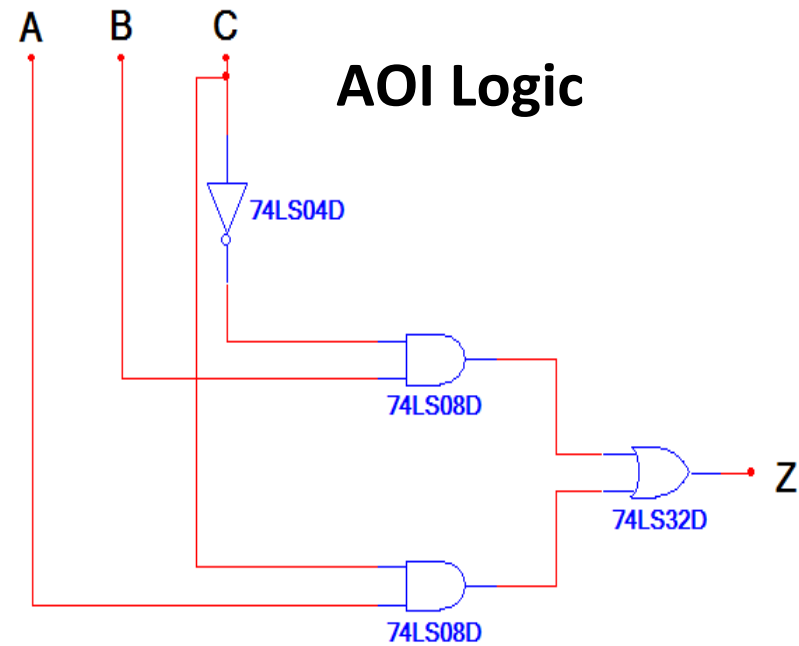

IC Type	Gates	Gate / IC	# ICs
74LS04	1	6	1
74LS08	2	4	1
74LS32	1	4	1
Total Number of ICs →			3

IC Type	Gates	Gate / IC	# ICs
74LS02	7	4	2
Total Number of ICs →			2

Unit II – Logic Gates & Logic Families



Logic Gates: Symbol, diode/transistor switch circuit and logical expression, truth table of basic gates (AND, OR, NOT), Universal gates (NAND, NOR) and special purpose gates (Ex-OR, Ex-NOR), Tristate Logic.



Boolean Algebra: Laws of Boolean algebra, Duality Theorem, De-Morgan's Theorem



Logic Families: Characteristics of Logic families: Noise Margin, Power Dissipation, Figure of merit, Fan in and Fan out, Speed of operation, Comparison TTL, CMOS, Types of TTL NAND gate.

Special Purpose Gate – Ex-OR Gate


- ✓ An Ex-OR gate is two input, one output logic circuit.
- ✓ The output assumes the logic 1 state, when one and only one of its two inputs assumes a logic 1 state.
- ✓ Under the conditions when both the inputs assume the logic 0 state or logic 1 state, the output assumes logic 0.

Ex-OR Gate



If input variables are represented by A and B and the output variable by Y the representation

for the output of this gate is as

 


$$Y = A \oplus B$$

$$Y = \overline{A}B + A\overline{B}$$

Logic Symbol

Logic Expression

Ex-OR Gate

 


$$Y = A \oplus B$$

0

Inputs		Output
A	B	$Y = A \oplus B$
0	0	0

Ex-OR Gate

 


$$Y=A\oplus B$$

1

Inputs		Output
A	B	$Y=A\oplus B$
0	0	0
0	1	1

Ex-OR Gate

 


$$Y=A\oplus B$$

1

Inputs		Output
A	B	$Y=A\oplus B$
0	0	0
0	1	1
1	0	1

Ex-OR Gate


 


$$Y=A\oplus B$$

0


Inputs		Output
A	B	$Y=A\oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

3 – Input Ex-OR Gate

  

INPUT			OUTPUT
A	B	C	$Y = A \oplus B \oplus C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 Ex-OR Gate IC – IC 7486 (Quad 2 I/P Ex-OR Gate)



Pin Configuration of IC 7486



This device contains four independent gates each of which performs the logic XOR function.

INPUTS		OUTPUT
A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

H = high level, L = low level

Function Table of IC 7486

Special Purpose Gate – Ex-NOR Gate


- ✓ An Ex-NOR gate is two input, one output logic circuit.
- ✓ The output assumes a logic 0 state, when one of the input assumes a logic 0 state and other a logic 1 state.
- ✓ The output assumes a logic 1 state only when both the inputs assume a logic 0 state or when both the inputs assume a logic state.

Ex-NOR Gate



If input variables are represented by A and B and the output variable by Y the representation

for the output of this gate is as

 


$$Y = A \odot B$$

$$Y = AB + AB$$

Logic Symbol


Logic Expression

Ex-NOR Gate

 


Inputs		Output
A	B	$Y = A \oplus B$
0	0	1

Ex-NOR Gate

 

Inputs		Output
A	B	$Y = A \oplus B$
0	0	1
0	1	0

Ex-NOR Gate

 


$Y = A \oplus B$

0

Inputs		Output
A	B	$Y = A \oplus B$
0	0	1
0	1	0
1	0	0

Ex-NOR Gate


 


$$Y = A \oplus B$$

1


Inputs		Output
A	B	$Y = A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

3 – Input Ex-NOR Gate

  

INPUT			OUTPUT
A	B	C	$Y=A \oplus B \oplus C$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Ex-NOR Gate IC – IC 74266

 

This device contains four independent gates each of which performs the logic XNOR function.

Pin Configuration of IC 74266

Unit II – Logic Gates & Logic Families



Logic Gates: Symbol, diode/transistor switch circuit and logical expression, truth table of basic gates (AND, OR, NOT), Universal gates (NAND, NOR) and special purpose gates (Ex-OR, Ex-NOR), Tristate Logic.



Boolean Algebra: Laws of Boolean algebra, Duality Theorem, De-Morgan's Theorem



Logic Families: Characteristics of Logic families: Noise Margin, Power Dissipation, Figure of merit, Fan in and Fan out, Speed of operation, Comparison TTL, CMOS, Types of TTL NAND gate.

Boolean Algebra



Boolean Algebra is used to analyze and simplify the digital (Logic) circuit.



Since it uses only the binary numbers i.e. 0 and 1 it is also called as “Binary Algebra” or “Logical Algebra”.

Boolean Algebra



The rules of Boolean Algebra are different from those of the conventional algebra.



It is invented by George Boole in the year 1854.

Unit II – Logic Gates & Logic Families



Logic Gates: Symbol, diode/transistor switch circuit and logical expression, truth table of basic gates (AND, OR, NOT), Universal gates (NAND, NOR) and special purpose gates (Ex-OR, Ex-NOR), Tristate Logic.



Boolean Algebra: Laws of Boolean algebra, Duality Theorem, De-Morgan's Theorem



Logic Families: Characteristics of Logic families: Noise Margin, Power Dissipation, Figure of merit, Fan in and Fan out, Speed of operation, Comparison TTL, CMOS, Types of TTL NAND gate.

Boolean Algebra



Axioms



Axioms or postulates of Boolean algebra are set of logical expressions that we accept without proof and upon which we can build a set of useful theorems.



Actually, axioms are nothing more than the definitions of the three basic logic operations that we have already discussed AND, OR and INVERT.

Boolean Algebra



Axioms

AND Operation

Axiom 1: $0.0=0$

Axiom 2: $0.1=0$

Axiom 3: $1.0=0$

Axiom 4: $1.1=1$

Boolean Algebra



Axioms

OR Operation

Axiom 5: $0+0=0$

Axiom 6: $0+1=1$

Axiom 7: $1+0=1$

Axiom 8: $1+1=1$

Boolean Algebra



Axioms

NOT Operation

$$\text{Axiom 9:} \quad \overline{1} = 0$$

$$\text{Axiom 10:} \quad \overline{0} = 1$$

Boolean Algebra



Inversion Law (or Complementation Law)

The term complement means to invert i.e. to change 0's to 1's and 1's to 0's.

Law 1: $\overline{1} = 0$

Law 2: $\overline{0} = 1$

Law 3: If $A=0$, then $\overline{A} = 1$

Law 4: If $A=1$, then $\overline{A} = 0$

Law 5: $\overline{\overline{A}} = A$ (Double Inversion Law)

Boolean Algebra



AND Laws

Law 1: $A \cdot 0 = 0$ Null Law

Law 2: $A \cdot 1 = A$ Identity Law

Law 3: $A \cdot A = A$

Law 4: $A \cdot A = 0$

Boolean Algebra



OR Laws

Law 1: $A + 0 = A$ Null Law

Law 2: $A + 1 = 1$ Identity Law

Law 3: $A + A = A$

Law 4: $A + \bar{A} = 1$

Boolean Algebra



Commutative Laws

$$\text{Law 1: } A+B = B+A$$



This Law states that, A OR B is the same as B OR A
i.e. the order in which the variables are ORed is
immaterial.




This means that it makes no difference which input
of an OR gate is connected to A and which to B.


Boolean Algebra

Proof:


$A+B$

 

Inputs		Output
A	B	$Y=A+B$
0	0	0
0	1	1
1	0	1
1	1	1

 

$B+A$

 

Inputs		Output
B	A	$Y=B+A$
0	0	0
0	1	1
1	0	1
1	1	1

Boolean Algebra



Commutative Laws



This law can be extended to any number of variables.
For example,

$$A+B+C = B+C+A = C+A+B = B+A+C$$

Boolean Algebra



Commutative Laws

$$\text{Law 2: } A.B = B.A$$




This Law states that, A AND B is the same as B AND A i.e. the order in which the variables are ANDed is immaterial.





This means that it makes no difference which input of an AND gate is connected to A and which to B.

Boolean Algebra

Proof:

 

Inputs		Output
A	B	$Y=A.B$
0	0	0
0	1	0
1	0	0
1	1	1

  

Inputs		Output
B	A	$Y=B.A$
0	0	0
0	1	0
1	0	0
1	1	1

Boolean Algebra



Commutative Laws



This law can be extended to any number of variables.
For example,

$$A.B.C = B.C.A = C.A.B = B.A.C$$

Boolean Algebra



Associative Laws

Law 1: $(A+B)+C = A+(B+C)$



A OR B ORed with C is the same as A ORed with B OR C.




This law states that the way the variables are grouped and ORed is immaterial.



Boolean Algebra

Proof:

$$(A+B)+C$$

 

$$A+(B+C)$$

  

A	B	C	A+B	(A+B)+C
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

A	B	C	B+C	A+(B+C)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	1
1	0	0	0	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Boolean Algebra



Associative Laws



This law can be extended to any number of variables. For example,

$$A+(B+C+D) = (A+B+C)+D = (A+B)+(C+D)$$

Boolean Algebra



Associative Laws

$$\text{Law 2: } (A.B).C = A.(B.C)$$



A AND B ANDed with C is the same as A ANDed with B AND C.




This law states that the way the variables are grouped and ANDed is immaterial.



Boolean Algebra

Proof:

$$(A.B).C$$

 

$$A.(B.C)$$

  

A	B	C	A.B	(A.B).C
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	1

A	B	C	B.C	A.(B.C)
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Boolean Algebra



Associative Laws



This law can be extended to any number of variables. For example,

$$A.(B.C.D) = (A.B.C).D = (A.B).(C.D)$$

Boolean Algebra



Distributive Laws

$$\text{Law 1: } A(B+C) = AB+AC$$




This law states that ORing of several variables and ANDing the result with a single variable is equivalent to ANDing that single variable with each of the several variables and then ORing the products.



Boolean Algebra

Proof:

$$A.(B+C)$$

 

$$AB+AC$$

  

A	B	C	B+C	A(B+C)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

A	B	C	AB	AC	AB+AC
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1



Distributive Laws



This law can be extended to any number of variables. For example,

$$ABC(D+E) = ABCD + ABCE$$

$$AB(CD+EF) = ABCD + ABEF$$

Boolean Algebra



Distributive Laws

$$\text{Law 2: } A+BC = (A+B).(A+C)$$





This law states that ANDing of several variables and ORing the result with a single variable is equivalent to ORing that single variable with each of the several variables and then ANDing the products.


Boolean Algebra

Proof:

$$A + (B \cdot C)$$

  

$$(A + B) \cdot (A + C)$$

 

A	B	C	BC	A+BC
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A	B	C	A+B	A+C	(A+B)·(A+C)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

Boolean Algebra



Redundant Literal Rule

$$\text{Law 1: } A + A \overline{B} = A + B$$




This law states that ORing of variable with the AND of the complement of that variable with another variable, is equal to the ORing of the two variables


Boolean Algebra

Proof:


$$A + \bar{A}B$$

 

$$A + B$$

 

A	B	$\bar{A}B$	$A + \bar{A}B$
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	1

 

A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Boolean Algebra



Redundant Literal Rule

Law 2: $A(A + B) = A.B$




This law states that ANDing of variable with the OR of the complement of that variable with another variable, is equal to the ANDing of the two variables


Boolean Algebra

Proof:


$$A(\bar{A} + B)$$

 

A	B	$\bar{A} + B$	$A(\bar{A} + B)$
0	0	1	0
0	1	1	0
1	0	0	0
1	1	1	1

 

$$A.B$$

 


A	B	$A.B$
0	0	0
0	1	0
1	0	0
1	1	1

Boolean Algebra



Idempotence Laws

Law 1: $A.A = A$

 


- ✓ Idempotence means the same value
- ✓ If $A=0$, then $A.A = 0.0 = 0 = A$
- ✓ If $A=1$, then $A.A = 1.1 = 1 = A$
- ✓ This law states that ANDing of a variable with itself is equal to that variable only.

Boolean Algebra



Idempotence Laws

Law 2: $A + A = A$

 

Idempotence means the same value



If $A=0$, then $A+A = 0+0 = 0 = A$



If $A=1$, then $A+A = 1+1 = 1 = A$



This law states that ORing of a variable with itself is equal to that variable only.

Boolean Algebra



Absorption Laws

$$\text{Law 1: } A + A.B = A$$



This law states that ORing of a variable with AND of that variable and another variable is equal to that variable itself.



Therefore,


$$A + A \cdot \text{Any Term} = A$$

Boolean Algebra

Proof:

$$A + A.B$$

$$A$$

 

A	B	$A.B$	$A + A.B$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

Boolean Algebra



Absorption Laws

Law 2: $A(A + B) = A$



This law states that ANDing of a variable with OR of that variable and another variable is equal to that variable itself.



Therefore,


$$A \cdot (A + \text{Any Term}) = A$$

Boolean Algebra

Proof:

$$A(A + B)$$

$$A$$

 

A	B	$A + B$	$A(A + B)$
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

Unit II – Logic Gates & Logic Families



Logic Gates: Symbol, diode/transistor switch circuit and logical expression, truth table of basic gates (AND, OR, NOT), Universal gates (NAND, NOR) and special purpose gates (Ex-OR, Ex-NOR), Tristate Logic.



Boolean Algebra: Laws of Boolean algebra, Duality Theorem,

De-Morgan's Theorem



Logic Families: Characteristics of Logic families: Noise Margin, Power Dissipation, Figure of merit, Fan in and Fan out, Speed of operation, Comparison TTL, CMOS, Types of TTL NAND gate.

Boolean Algebra



De-Morgan's Theorem

First Theorem:

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$



This theorem states that the complement of a sum of variables is equal to the product of their individual complements.






What it means is that the complement of two or more variables ORed together, is the same as the AND of the complements of each of the individual variables

Boolean Algebra




Proof: Logic Diagram

L.H.S.

   

NOR Gate

R.H.S.

   


Bubbled AND Gate

Boolean Algebra

Proof: Logic Table

$$\overline{A + B}$$

A	B	$A + B$	$\overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 

$$\overline{A} \cdot \overline{B}$$

A	B	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$
0	0	1	1	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	0



De-Morgan's Theorem



This law can be extended to any number of variables. For example,

$$\overline{A + B + C + D + \dots} = \overline{A} . \overline{B} . \overline{C} . \overline{D} . \dots$$
$$\overline{AB + CD + EFG + \dots} = \overline{AB} . \overline{CD} . \overline{EFG} . \dots$$



De-Morgan's Theorem

Second Theorem: $\overline{A.B} = \bar{A} + \bar{B}$



This theorem states that the complement of a product of variables is equal to the sum of their individual complements.






What it means is that the complement of two or more variables ANDed together, is the same as the OR of the complements of each of the individual variables




Boolean Algebra

Proof: Logic Diagram

L.H.S.

   

R.H.S.

   


NAND Gate

Bubbled OR Gate

Boolean Algebra

Proof:

$$\overline{A.B}$$

 

$$\overline{A} + \overline{B}$$

A	B	$A.B$	$\overline{A.B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A	B	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	1	1	1
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0



De-Morgan's Theorem



This law can be extended to any number of variables. For example,

$$\overline{A.B.C.D.....} = \bar{A} + \bar{B} + \bar{C} + \bar{D}.....$$

$$\overline{(AB)(CD)(EFG).....} = \overline{AB} + \overline{CD} + \overline{EFG} +$$

Unit II – Logic Gates & Logic Families



Logic Gates: Symbol, diode/transistor switch circuit and logical expression, truth table of basic gates (AND, OR, NOT), Universal gates (NAND, NOR) and special purpose gates (Ex-OR, Ex-NOR), Tristate Logic.



Boolean Algebra: Laws of Boolean algebra, **Duality Theorem**, De-Morgan's Theorem



Logic Families: Characteristics of Logic families: Noise Margin, Power Dissipation, Figure of merit, Fan in and Fan out, Speed of operation, Comparison TTL, CMOS, Types of TTL NAND gate.

Duality



Duality represents relation between expressions in positive logic system and expression in negative logic system.

Duality

- ✓ The distinction between positive and negative logic system is important.
- ✓ An OR gate in positive logic system becomes an AND gate in negative logic system and vice versa.
- ✓ Positive & negative logics thus give rise to a basic duality in all Boolean identities.

Duality

- ✓ When changing from one logic system to another 0 becomes 1 and 1 becomes 0.
- ✓ Furthermore, an AND gate becomes an OR gate and an OR gate becomes AND gate.

Duality

- ✓ Given Boolean identity, we can produce a dual identity by changing all '+' signs to '.' signs, all '.' signs to '+' signs and complementing all 0's and 1's.
- ✓ The variables are not complemented in this process.

Examples of Dual Identities

Sr. No.	Given Expression	Dual
1	$\overline{0} = 1$	$\overline{1} = 0$
2	$0.1 = 0$	$1+0=1$
3	$0.0=0$	$1+1=1$
4	$1.1=1$	$0+0=0$
5	$A.0=0$	$A+1=1$
6	$A.1= A$	$A+0=A$

Examples of Dual Identities

Sr. No.	Given Expression	Dual
7	$A.B = B.A$	$A+B=B+A$
8	$A.(B.C) = (A.B).C$	$A+(B+C) = (A+ B)+C$
9	$A.(B +C) = A.B + A.C$	$A+ BC = (A+ B)(A+C)$
10	$A.(A+ B) = A$	$A+AB=A$
11	$A.(A.B) = A.B$	$A+A+B= A+B$
12	$\overline{A.B} = \overline{A+B}$	$\overline{A+B} = \overline{A.B}$
13	$\overline{(A+ B)(A+ C)} = \overline{(A + B)(A+ C)}$	$\overline{AB+AC} = \overline{AB+AC}$

Example 1

Reduce the following Boolean Expression using Boolean Laws:

$$A.\bar{B} + \bar{A}.B + A.B + \bar{A}.\bar{B}$$

Example 1

Reduce the following Boolean Expression using Boolean Laws:

$$A.\bar{B} + \bar{A}.B + A.B + \bar{A}.\bar{B}$$

$$= A.\bar{B} + \bar{A}.B + A.B + \bar{A}.\bar{B}$$

$$= A.\bar{B} + A.B + \bar{A}.B + \bar{A}.\bar{B}$$

$$= A.(\bar{B} + B) + \bar{A}(\bar{B} + B) \quad (\because \bar{B} + B = 1)$$

$$= A + \bar{A} \quad (\because A + \bar{A} = 1)$$

$$= 1$$

$$A.\bar{B} + \bar{A}.B + A.B + \bar{A}.\bar{B} = 1$$

Example 2

Reduce the following Boolean Expression using Boolean Laws:

$$\overline{A}\overline{B}C + \overline{A}BC + ABC$$

Example 2

Reduce the following Boolean Expression using Boolean Laws:

$$\overline{A}\overline{B}C + \overline{A}BC + ABC$$

$$= \overline{A}\overline{B}C + \overline{A}BC + ABC$$

$$= \overline{A}\overline{B}C + BC(\overline{A} + A)$$

$$= \overline{A}\overline{B}C + BC \quad (\because A + \overline{A} = 1)$$

$$= C(\overline{A}\overline{B} + B)$$

$$= C(B + A)(\overline{B} + B) \quad (\because \text{Distributive Law})$$

$$= C(B + A) \quad (\because \overline{B} + B = 1)$$

$$= AC + BC$$

Example 3

Realize $Y=AB+AC$ using one OR gate and one AND gate

Example 3

Realize $Y=AB+AC$ using one OR gate and one AND gate

$$Y=AB+AC$$

A.B is one product term
Hence requires 1 AND gate

A.C is one product term
Hence requires 1 AND gate

A.C & A.B is one sum term
Hence requires 1 OR gate

Hence to implement $Y=AB+AC$ equation we require 2 AND gates and 1 OR gate


But we have to use only 1 AND gate and 1 OR gate

Hence simplification is necessary

Example 3

Continue.....

$$Y = AB + AC$$
$$= A(B+C)$$

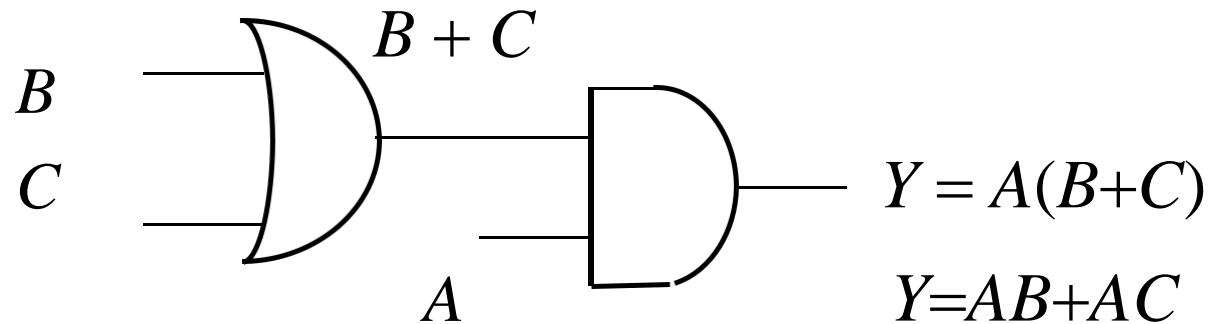

Example 4

Prove that:

$$\overline{A+AB} = A+B$$

Example 4

Prove that:

$$A + \bar{A}B = A + B$$

$$\begin{aligned}\text{L.H.S} &= A + \bar{A}B \\ &= A(1) + \bar{A}B \\ &= A(1 + B) + \bar{A}B \\ &= A + AB + \bar{A}B \\ &= A + B(A + \bar{A}) \\ &= A + B \quad \because (A + \bar{A} = 1)\end{aligned}$$

$$\text{L.H.S} = \text{R.H.S}$$

Example 5

Prove that:

$$(A + B)(A + \overline{B}) = A$$

Example 5

Prove that:

$$(A + B)(A + \bar{B}) = A$$

$$\text{L.H.S} = (A + B)(A + \bar{B})$$

$$= AA + A\bar{B} + AB + B\bar{B}$$

$$= A + \bar{A}B + AB + 0 \quad (\because AA=A, B\bar{B}=0)$$

$$= A + A(\bar{B} + B)$$

$$= A + A \quad (\because \bar{B} + B = 1)$$

$$= A \quad (\because A + A = A)$$

$$\text{L.H.S} = \text{R.H.S}$$

Example 6

With the help of Boolean Laws, Prove that:

$$(A + \bar{B} + AB)(A + B).\bar{A}\bar{B} = 0$$

Example 6

With the help of Boolean Laws, Prove that:

$$(A + \bar{B} + AB)(A + B).\bar{A}\bar{B} = 0$$

$$\text{L.H.S.} = (A + \bar{B} + AB)(A + \bar{B}).\bar{A}\bar{B}$$

$$= (A + \bar{B} + AB)(\bar{A}\bar{A}\bar{B} + \bar{A}\bar{B}\bar{B})$$

$$= (A + B + AB).(0) \quad (\because A.\bar{A}=0, B.\bar{B}=0)$$

$$= 0$$

$$\text{L.H.S} = \text{R.H.S}$$

Example 7

With the help of Boolean Laws, Prove that:

$$AB + \bar{A}B + \bar{A}\bar{B} = \bar{A} + B$$

Example 7

With the help of Boolean Laws, Prove that:

$$AB + \bar{A}B + \bar{A}\bar{B} = \bar{A} + B$$

$$\text{L.H.S.} = AB + \bar{A}B + \bar{A}\bar{B}$$

$$= \bar{A}B + \bar{A}\bar{B} + AB$$

$$= \bar{A}(B + \bar{B}) + AB$$

$$= \bar{A} + AB \quad (\because B + \bar{B} = 1)$$

$$= (A + \bar{A})(\bar{A} + B) \quad (\because \bar{A} + AB = (\bar{A} + A)(\bar{A} + B))$$

$$= 1.(\bar{A} + B) \quad (\because A + \bar{A} = 1)$$

$$= \bar{A} + B$$

$$\text{L.H.S.} = \text{R.H.S.}$$

Example 8

Simplify;

$$F = XY + XYZ + XYZ + XZY \quad -$$

Example 8

Simplify;

$$F = XY + XYZ + XYZ + XZY \quad -$$

$$F = XY + XYZ + XYZ + XZY \quad -$$

$$= XY + XYZ + X\bar{Z}Y \quad (\because XYZ + XYZ = XYZ)$$

$$= XY(1 + Z + \bar{Z})$$

$$= XY \quad (\because 1 + Z + \bar{Z} = 1)$$

$$= XY$$

Example 9

Prove that;

$$AB + ABC + A\overline{B} = A$$

Example 9

Prove that;

$$AB + ABC + \overline{A}B = A$$

$$L.H.S. = AB + ABC + \overline{A}B$$

$$= AB(1+C) + \overline{A}B$$

$$= AB + \overline{A}B \quad (\because 1+C=1)$$

$$= A(B + \overline{B})$$

$$= A \quad (\because B + \overline{B} = 1)$$

$$L.H.S = R.H.S$$